

Lab4
Zhiwen Wu
Robin (Haoran) Wang

a) Time usage: 8 hours each person

b) Table 1:

Cycle	reset	pc	Instr	branch	srca	srb	alurest	zero	pcsrc	Writedata	memwrite	read data
1	1	00	addi \$2,\$0,5 20020005	0	0	5	5	0	0	0	0	x
2	0	04	addi \$3,\$0,12 2003000c	0	0	c	c	0	0	0	0	x
3	0	08	addi \$7,\$3,-9 20067fff7	0	C	-9	3	0	0	0	0	x
4	0	0C	or \$4,\$7,\$2	0	3	5	7	0	0	5	0	X
5	0	10	and \$5,\$3,\$4	0	C	7	4	0	0	7	0	X
6	0	14	add \$5,\$5,\$4	0	4	7	6	0	0	7	0	X
7	0	18	beg \$5,\$7,end	1	b	3	8	0	0	3	0	x
8	0	1C	slr \$4,\$3,\$4	0	C	7	0	1	0	7	0	X
9	0	20	beg \$4,\$0,around	1	0	0	0	1	1	0	0	X
10	0	24	slr \$4,\$7,\$2	0	3	5	1	0	0	5	0	X
11	0	28	add \$7,\$4,\$5	0	1	b	c	0	0	6	0	X
12	0	2c	sub \$7,\$7,\$2	0	C	5	7	0	0	5	0	X
13	0	30	sw \$7,68C(\$3)	0	C	44	50	0	0	7	1	X
14	0	34	lw \$2,60C(\$0)	0	0	50	50	0	0	5	0	9
15	0	38	j end	0	0	0	0	1	0	0	0	X
16	0	3C	sw \$2,8a(\$0)	0	0	54	54	0	0	7	1	X

Table 1. First sixteen cycles of executing the test code of Fig. 7.60 in the textbook

c) Simulation waveforms



Fig.1 single cycle MIPS processor waveform


 


Fig.2 single cycle MIPS processor waveform

It writes the correct value to address 84: the value of writedata at the end is 00000007, as expected.

d)

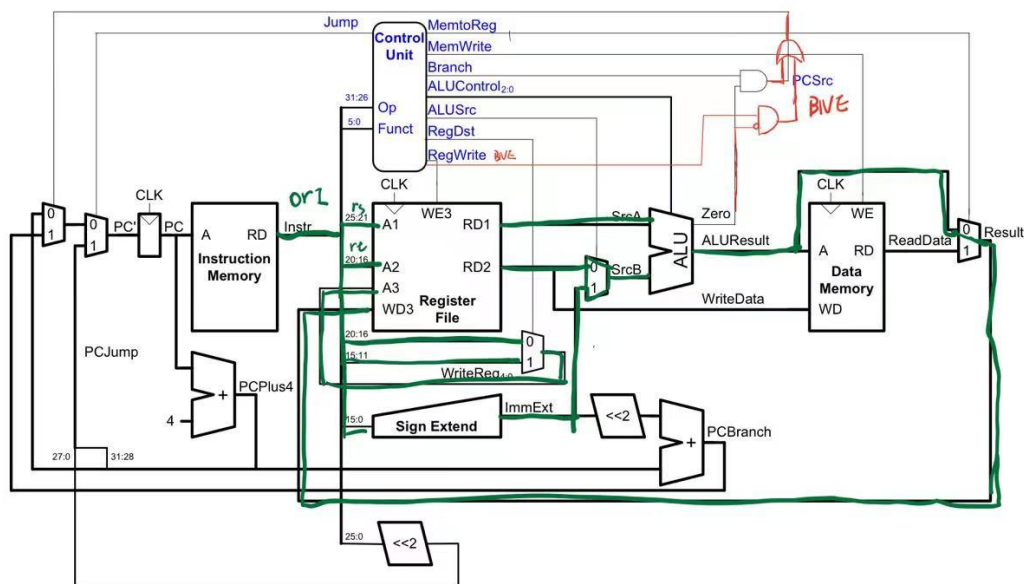

Single-cycle MIPS processor

Fig.3 data path and schematic of BNE and ORI implementation

e) Code: attached in the zip file, also linked at the end

f) Completed table 2 and 3

Table 2. Extended functionality for the main decoder:

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump	BN/E		
R-type	000000	1	1	0	0	0	0	10	0	0		
lw	100011	1	0	1	0	0	1	00	0	0		
sw	101011	0	X	1	0	1	X	00	0	0		
beq	000100	0	X	0	1	0	X	01	0	0		
addi	001000	1	0	1	0	0	0	00	0	0		
j	000010	0	X	X	X	0	X	XX	1	0		
ori	001101	1	0	1	0	0	0	11	0	0		
bne	000101	0	X	0	1	0	X	01	0	1		

Table 3. Extended functionality for the ALU decoder:

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at funct field
11	or

Fig.4 completed table 2 and 3

g) Memfile2.dat: attached in the zip file

12 lines (12 sloc) | 107 Byte:

```

1  34088000
2  20098000
3  350a8001
4  11090005
5  0128582a
6  15600001
7  08000009
8  01485022
9  350800ff
10 016a5820
11 01484022
12 ad680052

```

h) Image of simulation

 


Fig5. single cycle MIPS processor waveform with bne and ori

In the final sw instruction, the data value is 0000001 and the address is invalid because there are only 64 lines in the memory file.

Link to git repository: https://github.com/HBzhainan-wzw/ECE154A_Lab4

Link to google doc:

<https://docs.google.com/document/d/1h4wzuar8gBNxbDvFiJ4ZiycKzGo-aQtSozugiOzgYK4/edit>